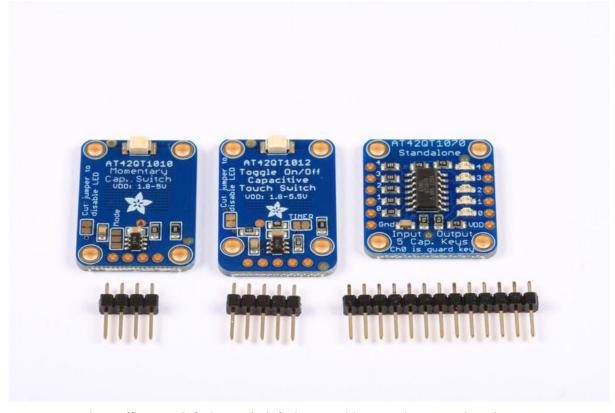


Adafruit Capacitive Touch Sensor Breakouts

Created by Bill Earl



https://learn.adafruit.com/adafruit-capacitive-touch-sensor-breakouts

Last updated on 2021-11-15 06:01:50 PM EST


© Adafruit Industries Page 1 of 24

Table of Contents

Overview	3
• Momentary	4
• Toggle	4
• 5-Pad Momentary	5
Assembly and Wiring	5
• Installing the Headers:	5
Position the header strips	5
Position the breakout	6
• And Solder	6
Wiring for Toggle and Momentary	7
Toggle Operation	7
Momentary Operation	8
• Other Options:	8
• LED Control	9
Speed vs. Power (Momentary Only)	9
• Timer (Toggle Only)	10
Connecting to your Circuit.	10
Simple Motor Control	11
Wiring for 5-pad Momentary	11
Adding Custom Touch Pads	12
Wire, Thread, Foil, Fabric, Paint	13
• Connections:	14
• Sensor Pads	15
Build a Touch Control Panel	15
Design your panel	16
• Cut the touch-pads	16
Attach the touch-pads	16
Attach the Wires	17
Adjust the Wires	17
• Install the Panel	18
And Test	19
Connect to your Circuit	20
Downloads	21
• Files	21
• AT42QT1010 Breakout	21
• AT42QT1012 Breakout	22
• AT42QT1070	23

© Adafruit Industries Page 2 of 24

Overview

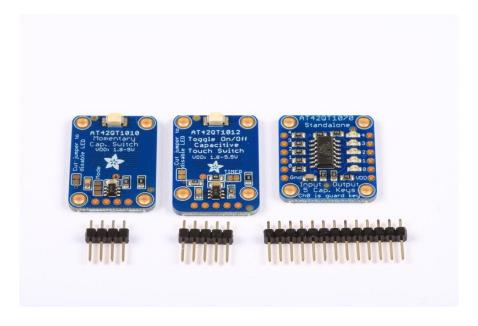


These breakout boards are a simple way to add capacitive touch to your project. Just power with 1.8 to 5.5VDC and touch the pad to activate the sensor. These touch switches interface easily to any project - with or without a microcontroller.

When a capacitive load (such as a human hand) is in close proximity to the sense-pad, the sensor detects the change in capacitance and activates the switch. Custom sense-pads can be made form nearly any conductive material and these sensors can detect touch through thin layers of non-conductive materials such as glass, plastic, fabric or even wood.


The breakouts come in three styles:


© Adafruit Industries Page 3 of 24

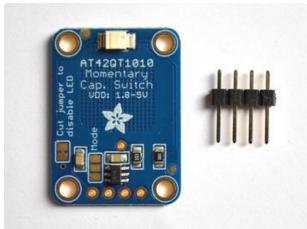



AT420T1010

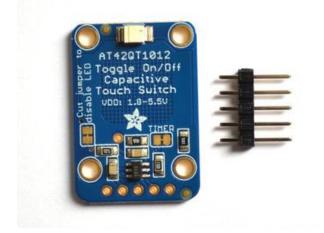

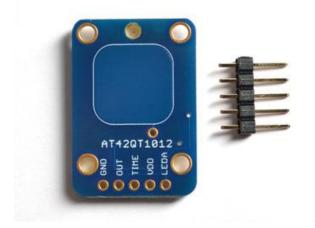

Momentary

This sensor has a built-in sense-pad and is active for as long as the sensor area is touched.


The sense-pad can be extended with wire and almost any conductive material.

Toggle

This sensor also has a built-in sense-pad. It becomes active when touched and remains active until it is touched again.


As with the momentary sensor, the sense-pad can be extended with wire and almost any conductive material.

©Adafruit Industries Page 4 of 24

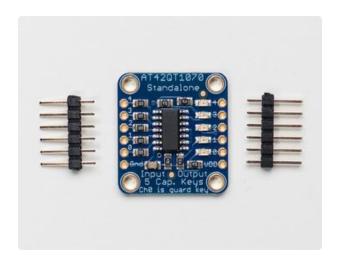

5-Pad Momentary

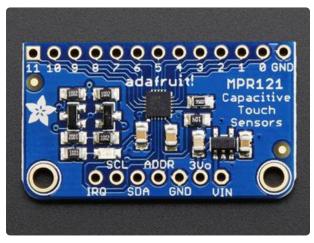This version combines 5 momentary switches into one breakout. There are 5 pins for attaching wires to up to 5 external sensor pads.




We also have a new 12-Key version with it's own tutorial over here! (https://adafru.it/dKH)

Assembly and Wiring

These breakouts come fully assembled. For use in a breadboard, you may want to take a couple minutes to install the included header strips:

Installing the Headers:

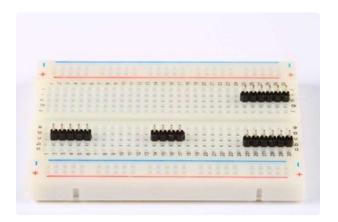
Install the headers by following these 3 easy steps. The photographs below show one of each sensor type.



Position the header strips


Plug them long-pins down into a breadboard to stabilize them for soldering.

© Adafruit Industries Page 5 of 24

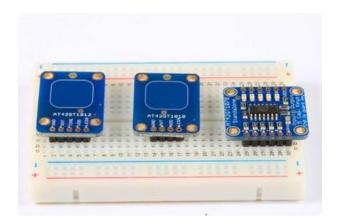


Position the breakout

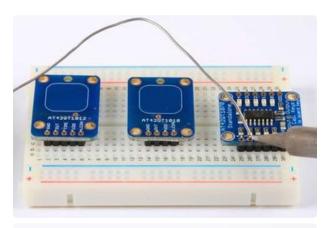Place the breakout board over the header pins.




And Solder

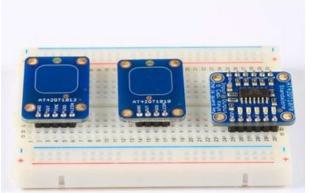Solder each pin for solid electrical contact.





© Adafruit Industries Page 6 of 24

Wiring for Toggle and Momentary

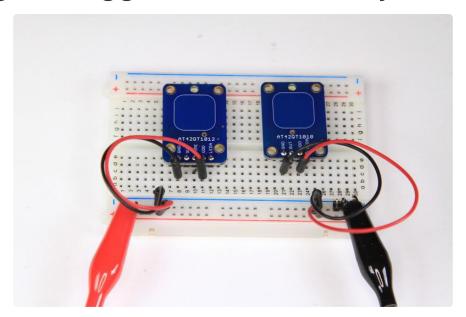

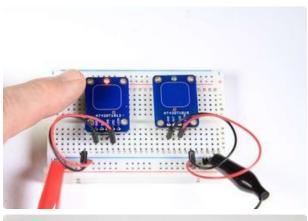These two breakouts are very similar and can be powered by anything from 1.8V to 5.5V DC. Simply connect Ground to GND and the positive voltage to VDD. The standalone sensors are fully functional without further connections.




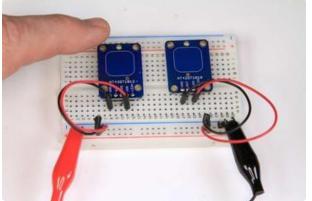

Toggle Operation


The Toggle version of the sensor turns on when you touch it once, then turns off when you touch it again. The on-board LED indicates the state of the switch.

© Adafruit Industries Page 7 of 24

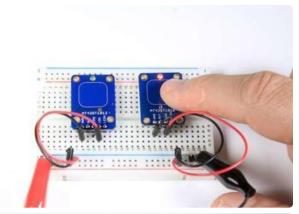



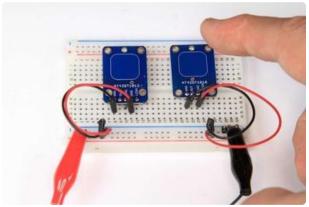
like a momentary touch sensor works just like a momentary switch. It is on when you touch it and off when you move away. The on-board LED indicates the state of the switch.



Other Options:

These sensors have several jumper configurable operating modes as described below:

© Adafruit Industries Page 8 of 24

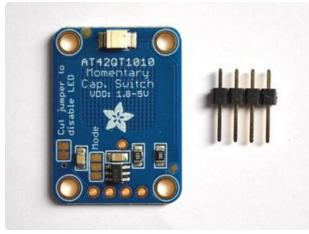




LED Control

The led indicators can be disabled for ultra-low power applications. To disable the LED, simply cut the jumper between the pads where indicated on the back of the breakout board.

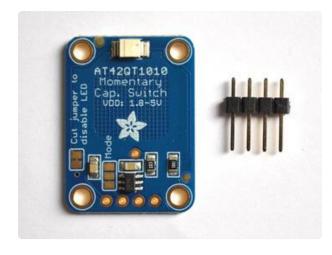With the jumper cut, the LED can be controlled externally via the LED pin on the header.



Speed vs. Power (Momentary Only)

The Momentary version can be configured for "Fast" mode (default) or low-power mode. Fast mode requires 0.5mA. Low Power mode requires just 50uA. To switch between the two, cut the jumper on one side of the "mode" pads and bridge the other side with a drop of solder.

© Adafruit Industries Page 9 of 24



Timer (Toggle Only)


By default, the toggle sensor is configured for infinte time-out. it will stay on until you touch the sensor to turn it off. It also supports a configurable time-out to turn off the output automatically after a delay. To select this mode, cut the 'TIMER' jumper and connect a resistor & capacitor to the TIME pin. For a circuit diagram and resistor/capacitor calculations, see page 13 of the datasheet (https://adafru.it/cgW).

You can also just connect TIME to Vdd and the chip will turn off approx 15 minutes after being turned on. Connect TIME to OUT and the chip will time-out approx one hour after being turned on.

Connecting to your Circuit.


The outputs of these touch switches are 'active high'. Use them like a positive logic signal, or a pushbutton that shorts to VCC.

© Adafruit Industries Page 10 of 24

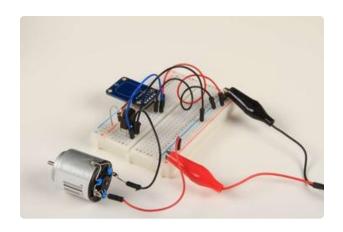


Simple Motor Control

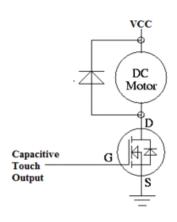You can use it just like a pushbutton or logic signal with a transistor or MOSFET to drive high-current loads like a DC motor.



Wiring for 5-pad Momentary

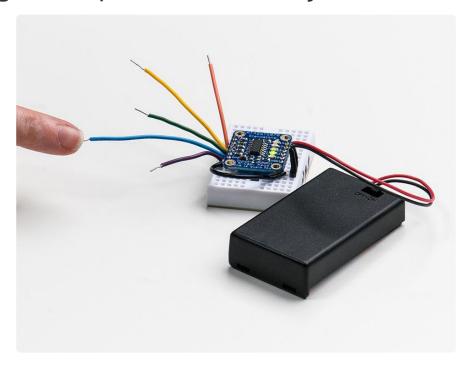


The 5-pin momentary breakout can be powered with anything from 1.8V to 5.5VDC. Just connect ground to GND and the positive voltage to VDD. This sensor does not

© Adafruit Industries Page 11 of 24

have built-in touch pads, but you can create your own pads in any size or shape from wire, foil or any other conductive material. Simply connect your touch-pads to each of the 5 sense pins. When you touch the pad, the corresponding LED on the other side will light up. The chip only detects one touch-pad at a time to prevent false readings.

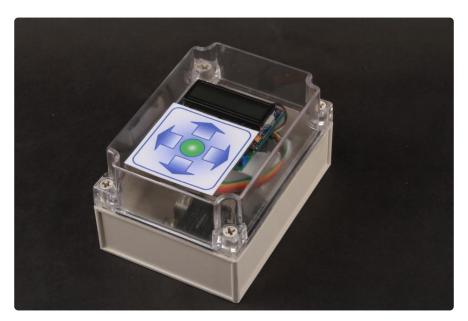5 touch inputs in one device makes this the perfect component for building your own custom capacitive touch panel!



Adding Custom Touch Pads

Custom touch pads are easy to make. You can use almost any conductive material:

© Adafruit Industries Page 12 of 24



Wire, Thread, Foil, Fabric, Paint

If it will conduct electricity, it will work as a touch sensor!






© Adafruit Industries Page 13 of 24





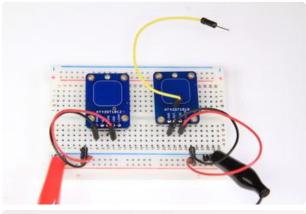





Connections:

The Toggle and Momentary boards have a solder hole located just below the sensor pad for attaching a wire to an external sensor.

The 5-pad breakout has pins numbered 0-4 on the left side of the board.

© Adafruit Industries Page 14 of 24

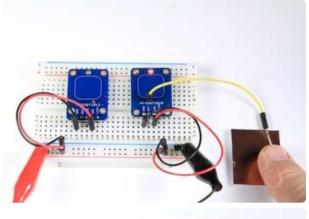

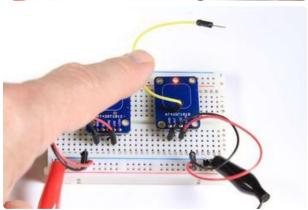

Sensor Pads

Attach the connecting wire to any conductive object or surface. That surface will become touch sensitive. Larger surfaces tend to be more sensitive. You will be able to sense through fabric, plastic glass and many other non-conductive materials.


Note that the wire will be touch sensitive too! Be sure to route any connecting wires away from areas where they might create an accidental touch input.

Build a Touch Control Panel




Capacitive touch sensors are a great way to add external controls to a waterproof enclosure. There is no need to drill holes or worry about gaskets and O-rings. These sensors will detect your touch right through the plastic case!

© Adafruit Industries Page 15 of 24

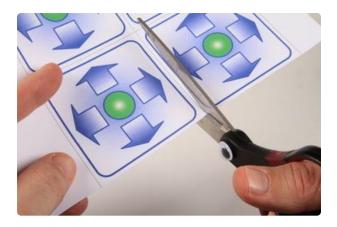


Design your panel

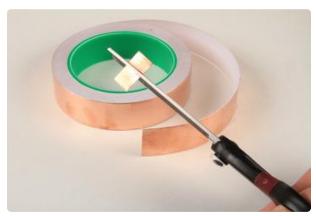You can draw it by hand, or with your favorite drawing tool and print it on some heavy card-stock.




Cut the touch-pads Cut pads from copper tape. About 1/2"

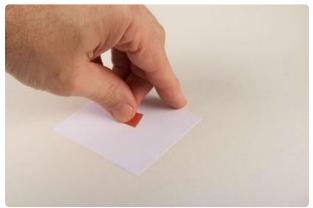Cut pads from copper tape. About 1/2" square is a good size for buttons on a touch-pad.




Attach the touch-pads

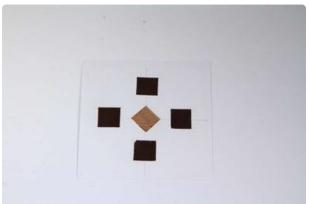Peel the release paper from the back of the copper tape and stick the touch-pads to be back of the panel so that they align with the buttons on the front.





© Adafruit Industries Page 16 of 24

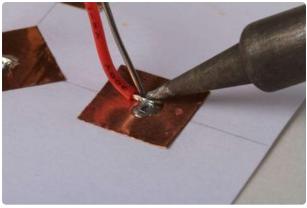


Attach the Wires

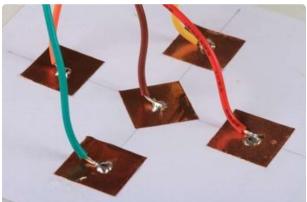
Solder wires to the copper touch-pads. For this example, I used a 6-conductor 0.1" socket cable (http://adafru.it/206) with one end cut off to simplify connections to the breakout.



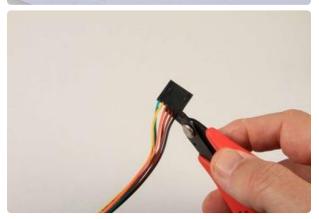


 

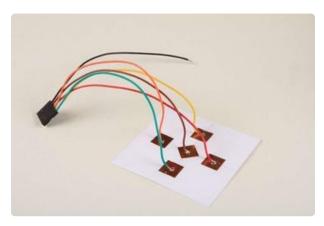
Bend the wires away from the panel. The wires will be touch-sensitive too. To prevent accidental false touches, we want to keep them away from the panel surface.




© Adafruit Industries Page 17 of 24

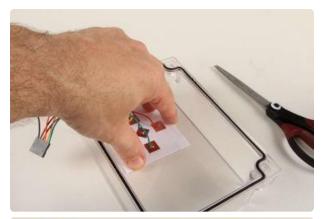


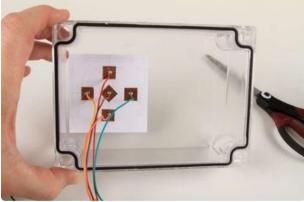Install the Panel
Tape the panel to the inside of the
polycarbonate cover using clear packing
tape.



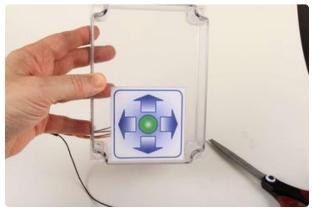

© Adafruit Industries Page 18 of 24

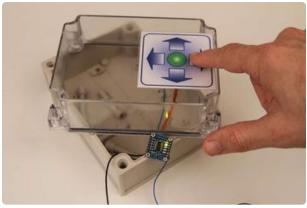




Connect the cable to the breakout.

Power it up and test your control panel.


Touching each button should cause a


different LED to light up.



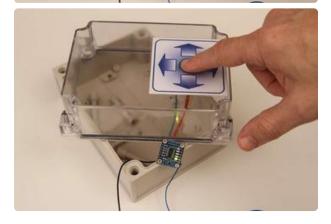

© Adafruit Industries Page 19 of 24

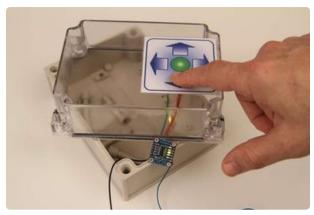

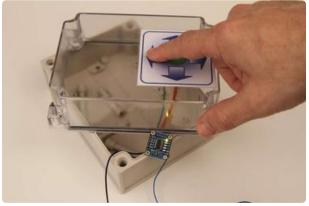




Connect to your Circuit

The output signals are 'active low', so they can replace any pushbutton that shorts to ground - such as the buttons on the RGB LCD shield. You can leave off the buttons and solder directly to the circled pads, or (if your shield is already built), just 'tack-solder' the wires to the legs of the buttons.

When you put it all together, you will have a completely sealed, touch sensitive control panel!

© Adafruit Industries Page 20 of 24

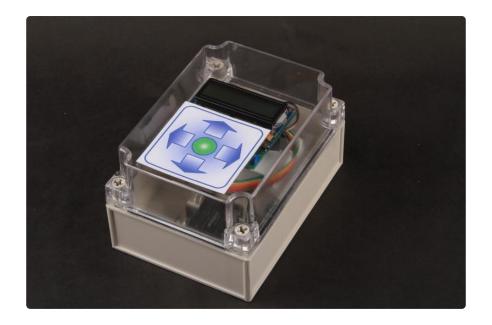


Downloads


Files

- AT42QT1070 Datasheet (https://adafru.it/rha)
- AT42QT1010 Datasheet (https://adafru.it/rhb)
- AT42QT1012 Datasheet (https://adafru.it/rhc)
- Objects for all in the Adafruit Fritzing Library (https://adafru.it/aP3)
- EagleCAD PCB files for all three in GitHub (https://adafru.it/rDr)


AT42QT1010 Breakout

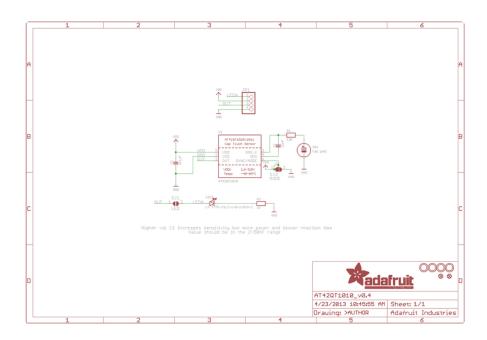


© Adafruit Industries Page 21 of 24

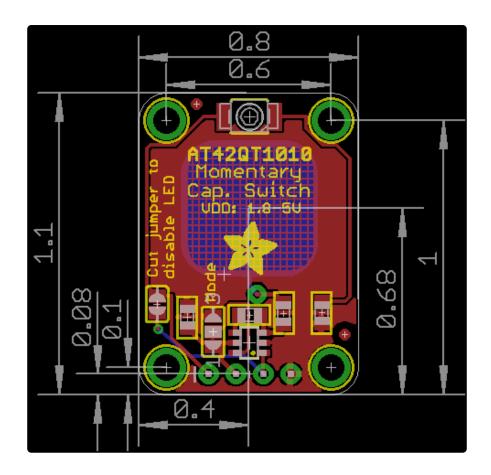


AT42QT1012 Breakout

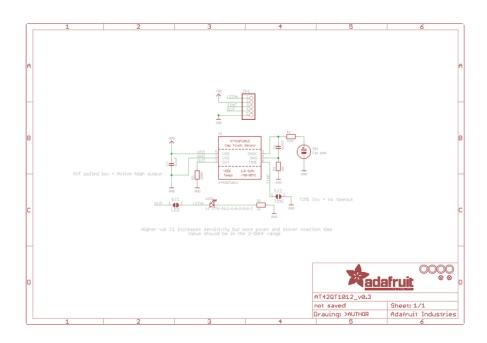


© Adafruit Industries Page 22 of 24

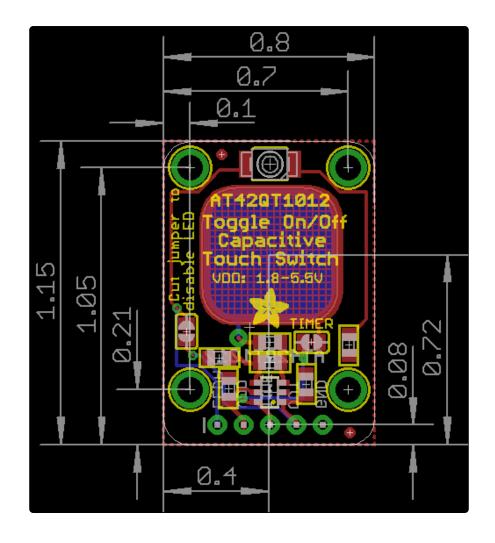

AT42QT1070

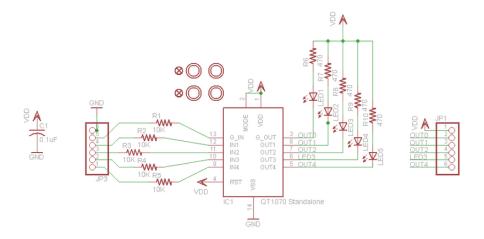

© Adafruit Industries Page 23 of 24

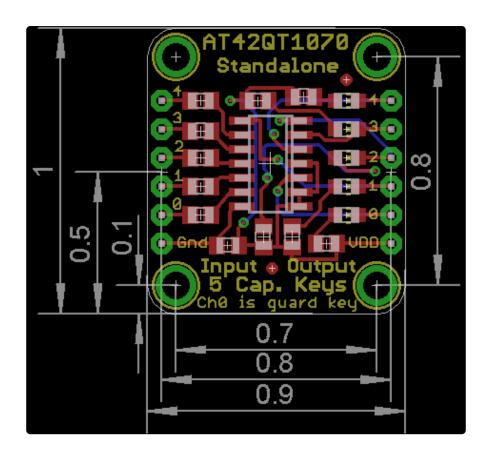

© Adafruit Industries Page 24 of 24

Mouser Electronics

Authorized Distributor

Click to View Pricing, Inventory, Delivery & Lifecycle Information:

Adafruit:

<u>1362</u> <u>1982</u>